

# Contents

<b>1</b>	<b>DC Systems</b>	<b>1</b>
1.1	Basic Quantities, Basic Laws	1
1.1.1	Electric Charge	1
1.1.2	Electric Current	1
1.1.3	Voltage and Potential	2
1.1.4	Ohm's Law	2
1.1.5	Resistance and Conductance	3
1.1.6	Temperature Dependence of Resistance	3
1.1.7	Inductance	4
1.1.8	Capacitance	4
1.1.9	Ideal Voltage Source	5
1.1.10	Ideal Current Source	5
1.1.11	Kirchhoff's Law	6
1.1.11.1	Kirchhoff's First Law (Current Law)	6
1.1.11.2	Kirchhoff's Second Law (Voltage Law)	6
1.1.12	Power and Energy	7
1.1.12.1	Energy and Power in a Resistor	7
1.1.12.2	Energy in an Inductor	8
1.1.12.3	Energy in a Capacitor	9
1.1.13	Efficiency	9
1.1.14	Maximum Power Transfer	10
1.2	Basic Circuits	11
1.2.1	Real Voltage and Current Sources	11
1.2.1.1	Real Voltage Source	11
1.2.1.2	Real Current Source	12
1.2.1.3	Voltage–Current Source Conversion	13
1.2.2	Circuit Elements in Series and Parallel	13
1.2.2.1	Series Combination of Resistors	13
1.2.2.2	Parallel Combination of Resistors	13
1.2.2.3	Series Combination of Conductances	14
1.2.2.4	Parallel Combination of Conductances	14
1.2.2.5	Series Combination of Inductances	15
1.2.2.6	Parallel Combination of Inductances	15
1.2.2.7	Series Combination of Capacitances	16
1.2.2.8	Parallel Combination of Capacitances	16
1.2.3	Star–Delta Transformation	17
1.2.4	Voltage and Current Divider	18
1.2.4.1	Voltage Divider	18
1.2.4.2	Current Divider	18
1.2.4.3	Capacitive and Inductive Dividers	19
1.2.5	<i>RC</i> and <i>RL</i> Combinations	19
1.2.5.1	Series Combination of <i>R</i> and <i>C</i> Driven by a Voltage Source	21
1.2.5.2	Series Combination of <i>R</i> and <i>C</i> Driven by a Current Source	21
1.2.5.3	Parallel Combination of <i>R</i> and <i>C</i> Driven by a Current Source	22
1.2.5.4	Parallel Combination of <i>R</i> and <i>C</i> Driven by a Voltage Source	22

1.2.5.5	Series Combination of $R$ and $L$ Driven by a Voltage Source	23
1.2.5.6	Series Combination of $R$ and $L$ Driven by a Current Source	23
1.2.5.7	Parallel Combination of $R$ and $L$ Driven by a Voltage Source	24
1.2.5.8	Parallel Combination of $R$ and $L$ Driven by a Current Source	24
1.2.6	RLC Combinations	25
1.2.6.1	Series Combination of $R$ , $L$ and $C$	26
1.3	Calculation Methods for Linear Circuits	29
1.3.1	Rules for Signs	29
1.3.2	Circuit Calculation with Mesh and Node Analysis	30
1.3.3	Superposition	31
1.3.4	Mesh Analysis	32
1.3.5	Node Analysis	33
1.3.6	Thévenin's and Norton's Theorem	33
1.3.6.1	Calculating a Load Current by Thévenin's Theorem	34
1.3.6.2	Calculating a Current Within a Network	36
1.4	Notation Index	37
1.5	Further Reading	38
<b>2</b>	<b>Electric Fields</b>	<b>39</b>
2.1	Electrostatic Fields	39
2.1.1	Coulomb's Law	39
2.1.2	Definition of Electric Field Strength	40
2.1.3	Voltage and Potential	41
2.1.4	Electrostatic Induction	42
2.1.5	Electric Displacement	43
2.1.6	Dielectrics	44
2.1.7	The Coulomb Integral	44
2.1.8	Gauss's Law of Electrostatics	45
2.1.9	Capacitance	46
2.1.10	Electrostatic Field at a Boundary	47
2.1.11	Overview: Fields and Capacitances of Different Geometric Configurations	48
2.1.12	Energy in an Electrostatic Field	49
2.1.13	Forces in an Electrostatic Field	50
2.1.13.1	Force on a Charge	50
2.1.13.2	Force at the Boundary	50
2.1.14	Overview: Characteristics of an Electrostatic Field	52
2.1.15	Relationship between the Electrostatic Field Quantities	53
2.2	Static Steady-State Current Flow	53
2.2.1	Voltage and Potential	53
2.2.2	Current	54
2.2.3	Electric Field Strength	54
2.2.4	Current Density	55
2.2.5	Resistivity and Conductivity	56
2.2.6	Resistance and Conductance	57
2.2.7	Kirchhoff's Laws	58
2.2.7.1	Kirchhoff's First Law (Current Law)	58
2.2.7.2	Kirchhoff's Second Law (Mesh Law)	59
2.2.8	Static Steady-State Current Flow at Boundaries	60

2.2.9	Overview: Fields and Resistances of Different Geometric Configurations . . . . .	61
2.2.10	Power and Energy in Static Steady-State Current Flow . . . . .	62
2.2.11	Overview: Characteristics of Static Steady-State Current Flow . . . . .	63
2.2.12	Relationship Between Quantities in Static Steady-State Current Flow . . . . .	64
2.3	Magnetic Fields . . . . .	64
2.3.1	Force on a Moving Charge . . . . .	65
2.3.2	Definition of Magnetic Flux Density . . . . .	66
2.3.3	Biot–Savart’s Law . . . . .	68
2.3.4	Magnetic Field Strength . . . . .	69
2.3.5	Magnetic Flux . . . . .	70
2.3.6	Magnetic Voltage and Ampere’s Law . . . . .	71
2.3.7	Magnetic Resistance, Magnetic Conductance, Inductance . . . . .	73
2.3.8	Materials in a Magnetic Field . . . . .	74
2.3.8.1	Ferromagnetic Materials . . . . .	75
2.3.9	Magnetic Fields at Boundaries . . . . .	77
2.3.10	The Magnetic Circuit . . . . .	78
2.3.11	Magnetic Circuit with a Permanent Magnet . . . . .	80
2.3.12	Overview: Inductances of Different Geometric Configurations . . . . .	82
2.3.13	Induction . . . . .	83
2.3.13.1	Induction in a Moving Electrical Conductor . . . . .	83
2.3.13.2	Faraday’s Law of Induction . . . . .	84
2.3.13.3	Self-Induction . . . . .	87
2.3.14	Mutual Induction . . . . .	88
2.3.15	Transformer Principle . . . . .	90
2.3.16	Energy in a Magnetic Field . . . . .	90
2.3.16.1	Energy in a Magnetic Circuit with an Air Gap . . . . .	91
2.3.17	Forces in a Magnetic Field . . . . .	92
2.3.17.1	Force on a Current-Carrying Conductor . . . . .	92
2.3.17.2	Force at the Boundaries . . . . .	93
2.3.18	Overview: Characteristics of a Magnetic Field . . . . .	94
2.3.19	Relationship between the Magnetic Field Quantities . . . . .	95
2.4	Maxwell’s Equations . . . . .	95
2.5	Notation Index . . . . .	96
2.6	Further Reading . . . . .	98

**3 AC Systems 99**

3.1	Mathematical Basics of AC . . . . .	99
3.1.1	Sine and Cosine Functions . . . . .	99
3.1.1.1	Addition of Sinusoidal Waveforms . . . . .	100
3.1.2	Complex Numbers . . . . .	101
3.1.2.1	Complex Arithmetic . . . . .	102
3.1.2.2	Representation of Complex Numbers . . . . .	103
3.1.2.3	Changing Between Different Representations . . . . .	105
3.1.3	Complex Calculus . . . . .	105
3.1.3.1	Complex Addition and Subtraction . . . . .	105
3.1.3.2	Multiplication of Complex Numbers . . . . .	106
3.1.4	Overview: Complex Number Arithmetic . . . . .	107
3.1.5	The Complex Exponential Function . . . . .	107
3.1.5.1	Exponential Function with Imaginary Exponents . . . . .	108
3.1.5.2	Exponential Function with Complex Exponents . . . . .	108
3.1.6	Trigonometric Functions with Complex Arguments . . . . .	109
3.1.7	From Sinusoidal Waveforms to Phasors . . . . .	109
3.1.7.1	Complex Magnitude . . . . .	109

	3.1.7.2	Relationship Between Sinusoidal Waveforms and Phasors	110
	3.1.7.3	Addition and Subtraction of Phasors	111
3.2		Sinusoidal Waveforms	112
	3.2.1	Characteristics of Sinusoidal Waveforms	113
	3.2.2	Characteristics of Nonsinusoidal Waveforms	115
3.3		Complex Impedance and Admittance	116
	3.3.1	Impedance	116
	3.3.2	Complex Impedance of Passive Components	118
		3.3.2.1 Resistor	118
		3.3.2.2 Inductor	118
		3.3.2.3 Capacitor	118
	3.3.3	Admittance	119
	3.3.4	Complex Admittance of Passive Components	120
	3.3.5	Overview: Complex Impedance	121
3.4		Impedance of Passive Components	122
3.5		Combinations of Passive Components	123
	3.5.1	Series Combinations	123
		3.5.1.1 General Case	123
		3.5.1.2 Resistor and Inductor in Series	124
		3.5.1.3 Resistor and Capacitor in Series	125
		3.5.1.4 Resistor, Inductor and Capacitor in Series	126
	3.5.2	Parallel Combinations	128
		3.5.2.1 General Case	128
		3.5.2.2 Resistor and Inductor in Parallel	129
		3.5.2.3 Resistor and Capacitor in Parallel	130
		3.5.2.4 Resistor, Inductor and Capacitor in Parallel	132
	3.5.3	Overview of Series and Parallel Circuits	134
3.6		Network Transformations	135
	3.6.1	Transformation from Parallel to Series Circuits and Vice Versa	135
	3.6.2	Star–Delta (Wye–Delta) and Delta–Star (Delta–Wye) Transformations	137
	3.6.3	Circuit Duality	139
3.7		Simple Networks	140
	3.7.1	Complex Voltage and Current Division	140
	3.7.2	Loaded Complex Voltage Divider	142
	3.7.3	Impedance Matching	143
	3.7.4	Voltage Divider with Defined Input and Output Resistances	145
	3.7.5	Phase-Shifting Circuits	146
		3.7.5.1 RC Phase Shifter	146
		3.7.5.2 Alternative Phase-Shifting Circuits	148
	3.7.6	AC Bridges	149
		3.7.6.1 Balancing Condition	149
		3.7.6.2 Application: Measurement Technique	150
3.8		Power in AC Circuits	151
	3.8.1	Instantaneous Power	151
		3.8.1.1 Power in a Resistance	151
		3.8.1.2 Power in a Reactive Element	151
	3.8.2	Average Power	152
		3.8.2.1 Real Power	153
		3.8.2.2 Reactive Power	154
		3.8.2.3 Apparent Power	155
	3.8.3	Complex Power	155
	3.8.4	Overview: AC Power	156

3.8.5	Reactive Current Compensation . . . . .	156
3.9	Three-Phase Supplies . . . . .	158
3.9.1	Polyphase Systems . . . . .	158
3.9.2	Three-Phase Systems . . . . .	159
3.9.2.1	Properties of the Complex Operator $a$ . . . . .	160
3.9.3	Delta-Connected Generators . . . . .	161
3.9.4	Star-Connected Generators . . . . .	162
3.10	Overview: Symmetrical Three-Phase Systems . . . . .	164
3.10.1	Power in a Three-Phase System . . . . .	165
3.11	Notation Index . . . . .	166
3.12	Further Reading . . . . .	167
<b>4</b>	<b>Current, Voltage and Power Measurement</b>	<b>169</b>
4.1	Electrical Measuring Instruments . . . . .	169
4.1.1	Moving-Coil Instrument . . . . .	169
4.1.2	Ratiometer Moving-Coil Instrument . . . . .	169
4.1.3	Electrodynamic Instrument . . . . .	170
4.1.4	Moving-Iron Instrument . . . . .	171
4.1.5	Other Instruments . . . . .	171
4.1.6	Overview: Electrical Instruments . . . . .	173
4.2	Measurement of DC Current and Voltage . . . . .	174
4.2.1	Moving-Coil Instrument . . . . .	174
4.2.2	Range Extension for Current Measurements . . . . .	174
4.2.3	Range Extension for Voltage Measurements . . . . .	175
4.2.4	Overload Protection . . . . .	176
4.2.5	Systematic Measurement Errors in Current and Voltage Measurement . . . . .	176
4.3	Measurement of AC Voltage and AC Current . . . . .	177
4.3.1	Moving-Coil Instrument with Rectifier . . . . .	177
4.3.2	Moving-Iron Instruments . . . . .	179
4.3.3	Measurement Range Extension Using an Instrument Transformer . . . . .	179
4.3.4	RMS Measurement . . . . .	180
4.4	Power Measurement . . . . .	181
4.4.1	Power Measurement in a DC Circuit . . . . .	181
4.4.2	Power Measurement in an AC Circuit . . . . .	182
4.4.2.1	Three-Voltmeter Method . . . . .	183
4.4.2.2	Power Factor Measurement . . . . .	184
4.4.3	Power Measurement in a Multiphase System . . . . .	185
4.4.3.1	Measurement of the Real Power in a Multiphase System . . . . .	185
4.4.3.2	Measurement of the Reactive Power in a Multiphase System . . . . .	186
4.5	Measurement Errors . . . . .	187
4.5.1	Systematic and Random Errors . . . . .	187
4.5.2	Guaranteed Error Limits . . . . .	188
4.6	Overview: Symbols on Measurement Instruments . . . . .	188
4.7	Overview: Measurement Methods . . . . .	190
4.8	Notation Index . . . . .	190
4.9	Further Reading . . . . .	191
<b>5</b>	<b>Networks at Variable Frequency</b>	<b>192</b>
5.1	Linear Systems . . . . .	192
5.1.1	Transfer Function, Amplitude and Phase Response . . . . .	192
5.2	Filters . . . . .	194

5.2.1	Low-Pass Filter	195
5.2.2	High-Pass Filter	195
5.2.3	Bandpass Filter	196
5.2.4	Stop-Band Filter	197
5.2.5	All-Pass Filter	197
5.3	Simple Filters	197
5.3.1	Low-Pass Filter	197
5.3.1.1	Rise Time	198
5.3.2	Frequency Normalisation	199
5.3.2.1	Approximation of the Magnitude Response	200
5.3.3	High-Pass Filter	200
5.3.3.1	Approximation of the Magnitude Response	202
5.3.4	Higher-Order Filters	202
5.3.5	Bandpass Filter	204
5.3.6	Filter Realisation	206
5.4	Notation Index	206
5.5	Further Reading	207
<b>6</b>	<b>Signals and Systems</b>	<b>208</b>
6.1	Signals	208
6.1.1	Definitions	208
6.1.2	Symmetry Properties of Signals	209
6.2	Fourier Series	210
6.2.1	Trigonometric Form	210
6.2.1.1	Symmetry Properties	211
6.2.2	Amplitude–Phase Form	211
6.2.3	Exponential Form	212
6.2.3.1	Symmetry Properties	213
6.2.4	Overview: Fourier Series Representations	213
6.2.5	Useful Integrals for the Calculation of Fourier Coefficients	214
6.2.6	Useful Fourier Series	215
6.2.7	Application of the Fourier Series	217
6.2.7.1	Spectrum of a Rectangular Signal	217
6.2.7.2	Spectrum of a Sawtooth Signal	218
6.2.7.3	Spectrum of a Composite Signal	219
6.3	Systems	220
6.3.1	System Properties	220
6.3.1.1	Linear Systems	220
6.3.1.2	Causal Systems	221
6.3.1.3	Time-Invariant Systems	221
6.3.1.4	Stable Systems	222
6.3.1.5	LTI Systems	222
6.3.2	Elementary Signals	222
6.3.2.1	The Step Function	222
6.3.2.2	The Rectangular Pulse	222
6.3.2.3	The Triangular Pulse	223
6.3.2.4	The Gaussian Pulse	223
6.3.2.5	The Impulse Function (Delta Function)	224
6.3.3	Shifting and Scaling of Time Signals	225
6.3.4	System Responses	226
6.3.4.1	Impulse Response	226
6.3.4.2	Step Response	227
6.3.4.3	System Response to Arbitrary Input Signals	228
6.3.4.4	Rules of Convolution	228

6.3.4.5	Transfer Function . . . . .	230
6.3.4.6	System Response Calculation in the Frequency Domain . . . . .	230
6.3.5	Impulse and Step Response Calculation . . . . .	231
6.3.5.1	Normalisation of Circuits . . . . .	231
6.3.5.2	Impulse and Step Response of First-Order Systems . . . . .	232
6.3.5.3	Impulse and Step Response of Second-Order Systems . . . . .	234
6.3.6	Ideal Systems . . . . .	236
6.3.6.1	Distortion-Free Systems . . . . .	236
6.3.6.2	Ideal Low-Pass Filter . . . . .	238
6.3.6.3	Ideal Bandpass Filter . . . . .	240
6.4	Fourier Transforms . . . . .	241
6.4.1	Principle . . . . .	241
6.4.2	Definition . . . . .	242
6.4.3	Representation of the Fourier Transform . . . . .	243
6.4.3.1	Symmetry Properties . . . . .	244
6.4.4	Overview: Properties of the Fourier Transform . . . . .	244
6.4.5	Fourier Transforms of Elementary Signals . . . . .	245
6.4.5.1	Spectrum of the Delta Function . . . . .	245
6.4.5.2	Spectrum of the Signum and the Step Functions . . . . .	246
6.4.5.3	Spectrum of the Rectangular Pulse . . . . .	247
6.4.5.4	Spectrum of the Triangular Pulse . . . . .	247
6.4.5.5	Spectrum of the Gaussian Pulse . . . . .	248
6.4.5.6	Spectrum of Harmonic Functions . . . . .	249
6.4.6	Summary of Fourier Transforms . . . . .	250
6.5	Nonlinear Systems . . . . .	253
6.5.1	Definition . . . . .	253
6.5.2	Characterisation of Nonlinear Systems . . . . .	253
6.5.2.1	Characteristic Equation . . . . .	253
6.5.2.2	Total Harmonic Distortion . . . . .	254
6.5.2.3	Signal-to-Intermodulation Ratio . . . . .	255
6.6	Notation Index . . . . .	258
6.7	Further Reading . . . . .	259
<b>7</b>	<b>Analogue Circuit Design</b> . . . . .	<b>261</b>
7.1	Methods of Analysis . . . . .	261
7.1.1	Linearisation at the Operating Point . . . . .	261
7.1.2	AC Equivalent Circuit . . . . .	262
7.1.3	Input and Output Impedance . . . . .	263
7.1.3.1	Determination of the Input Impedance . . . . .	263
7.1.3.2	Determination of the Output Impedance . . . . .	263
7.1.3.3	Combination of Two-Terminal Networks . . . . .	264
7.1.4	Two-Port Networks . . . . .	265
7.1.4.1	Two-Port Network Equations . . . . .	265
7.1.4.2	Hybrid Parameters ( <i>h</i> -Parameters) . . . . .	265
7.1.4.3	Admittance Parameters ( <i>y</i> -Parameters) . . . . .	266
7.1.5	Block Diagrams . . . . .	267
7.1.5.1	Calculation Rules for Block Diagrams . . . . .	268
7.1.6	Bode Plot . . . . .	269
7.2	Silicon and Germanium Diodes . . . . .	269
7.2.1	Current–Voltage Characteristic of Si and Ge Diodes . . . . .	270
7.2.2	Temperature Dependency of the Threshold Voltage . . . . .	270
7.2.3	Dynamic Resistance (Differential Resistance) . . . . .	271
7.3	Small-Signal Amplifier with Bipolar Transistors . . . . .	271
7.3.1	Transistor Characteristics . . . . .	272

7.3.1.1	Symbols, Voltages and Currents for Bipolar Transistors .	272
7.3.1.2	Output Characteristics . . . . .	272
7.3.1.3	Transfer Characteristic . . . . .	273
7.3.1.4	Input Characteristic . . . . .	273
7.3.1.5	Static Current Gain $\beta_{DC}$ . . . . .	274
7.3.1.6	Differential Current Gain $\beta$ . . . . .	274
7.3.1.7	Transconductance $g_m$ . . . . .	275
7.3.1.8	Thermal Voltage Drift . . . . .	275
7.3.1.9	Differential Input Resistance $r_{BE}$ . . . . .	275
7.3.1.10	Differential Output Resistance $r_{CE}$ . . . . .	275
7.3.1.11	Reverse Voltage-Transfer Ratio $A_r$ . . . . .	276
7.3.1.12	Unity Gain and Critical Frequencies . . . . .	276
7.3.2	Equivalent Circuits . . . . .	276
7.3.2.1	Static Equivalent Circuit . . . . .	276
7.3.2.2	AC Equivalent Circuit . . . . .	277
7.3.2.3	The Giacoletto Equivalent Circuit . . . . .	278
7.3.3	Darlington Pair . . . . .	278
7.3.3.1	Pseudo-Darlington Pair . . . . .	279
7.3.4	Basic Circuits with Bipolar Transistors . . . . .	280
7.3.5	Common-Emitter Circuit . . . . .	280
7.3.5.1	Common-Emitter Circuit Two-Port Network Equations .	281
7.3.5.2	Common-Emitter AC Equivalent Circuit . . . . .	282
7.3.5.3	Common-Emitter Circuit Input Impedance . . . . .	283
7.3.5.4	Common-Emitter Circuit Output Impedance . . . . .	284
7.3.5.5	Common-Emitter Circuit AC Voltage Gain . . . . .	285
7.3.5.6	Operating Point Biasing . . . . .	286
7.3.5.7	Operating Point Stabilisation . . . . .	288
7.3.5.8	Load Line . . . . .	290
7.3.5.9	Common-Emitter Circuit at High Frequencies . . . . .	291
7.3.6	Common-Collector Circuit (Emitter Follower) . . . . .	291
7.3.6.1	Common-Collector AC Equivalent Circuit . . . . .	292
7.3.6.2	Common-Collector Circuit Input Impedance . . . . .	293
7.3.6.3	Common-Collector Circuit Output Impedance . . . . .	293
7.3.6.4	Common-Collector Circuit AC Current Gain . . . . .	294
7.3.6.5	Common-Collector Circuit at High Frequencies . . . . .	294
7.3.7	Common-Base Circuit . . . . .	294
7.3.7.1	Common-Base AC Equivalent Circuit . . . . .	295
7.3.7.2	Common-Base Circuit Input Impedance . . . . .	295
7.3.7.3	Common-Base Circuit Output Impedance . . . . .	295
7.3.7.4	Common-Base Circuit AC Voltage Gain . . . . .	296
7.3.7.5	Common-Base Circuit at High Frequencies . . . . .	296
7.3.8	Overview: Basic Bipolar Transistor Circuits . . . . .	296
7.3.9	Bipolar Transistor Current Sources . . . . .	296
7.3.10	Bipolar Transistor Differential Amplifier . . . . .	298
7.3.10.1	Differential Mode Gain . . . . .	300
7.3.10.2	Common-Mode Gain . . . . .	301
7.3.10.3	Common-Mode Rejection Ratio . . . . .	301
7.3.10.4	Differential Amplifier Input Impedance . . . . .	302
7.3.10.5	Differential Amplifier Output Impedance . . . . .	302
7.3.10.6	Offset Voltage of the Differential Amplifier . . . . .	302
7.3.10.7	Differential Amplifier Offset Current . . . . .	302
7.3.10.8	Input Offset Voltage Drift . . . . .	302
7.3.10.9	Differential Amplifier Examples . . . . .	303
7.3.11	Overview: Bipolar Transistor Differential Amplifiers . . . . .	304



7.3.12	Current Mirror	304
7.3.12.1	Current Mirror Variations	305
7.4	Field-Effect Transistor Small-Signal Amplifiers	305
7.4.1	Transistor Characteristics and Ratings	305
7.4.1.1	Symbols, Voltages and Currents for Field-Effect Transistors	305
7.4.1.2	JFET Characteristic Curves	307
7.4.1.3	IGFET Characteristic Curves	307
7.4.1.4	Transconductance	308
7.4.1.5	Dynamic Output Resistance	309
7.4.1.6	Input Impedance	309
7.4.2	Equivalent Circuit	309
7.4.2.1	Equivalent Circuit for Low Frequencies	309
7.4.2.2	Equivalent Circuit for High Frequencies	310
7.4.2.3	Critical Frequency of Transconductance	310
7.4.3	Basic Circuits using Field-Effect Transistors	310
7.4.4	Common-Source Circuit	310
7.4.4.1	Common-Source Two-Port Parameters	311
7.4.4.2	AC Equivalent Circuit of the Common-Source Circuit	312
7.4.4.3	Input Impedance of the Common-Source Circuit	313
7.4.4.4	Output Impedance of the Common-Source Circuit	313
7.4.4.5	AC Voltage Gain	314
7.4.4.6	Operating-Point Biasing	314
7.4.4.7	Common-Drain Circuit, Source Follower	316
7.4.4.8	AC Equivalent Circuit of the common-drain Circuit	316
7.4.4.9	Input Impedance of the Common-Drain Circuit	317
7.4.4.10	Output Impedance of the Common-Drain Circuit	317
7.4.4.11	Voltage Gain of the Common-Drain Circuit	317
7.4.4.12	Common-Drain Circuit at High Frequencies	317
7.4.5	Common-Gate Circuit	317
7.4.5.1	Input Impedance of the Common-Gate Circuit	318
7.4.5.2	Output Impedance of the Common-Gate Circuit	318
7.4.5.3	Voltage Gain of the Common-Gate Circuit	318
7.4.6	Overview: Basic Circuits using Field-Effect Transistors	318
7.4.7	FET Current Source	319
7.4.8	Differential Amplifier with Field-Effect Transistors	319
7.4.8.1	Differential Mode Gain	320
7.4.8.2	Common-Mode Gain	320
7.4.8.3	Common-Mode Rejection Ratio	321
7.4.8.4	Input Impedance	321
7.4.8.5	Output Impedance	321
7.4.9	Overview: Differential Amplifier with FETs	321
7.4.10	Controllable Resistor FETs	321
7.5	Negative Feedback	322
7.5.1	Feedback Topologies	324
7.5.2	Influence of Negative Feedback on the Input and Output Impedance	326
7.5.2.1	Input and Output Impedance of the Four Kinds of Feedback	327
7.5.3	Influence of Negative Feedback on Frequency Response	327
7.5.4	Stability of Systems with Negative Feedback	328
7.6	Operational Amplifiers	329
7.6.1	Characteristics of the Operational Amplifier	330
7.6.1.1	Output Voltage Swing	330

7.6.1.2	Offset Voltage	330
7.6.1.3	Offset Voltage Drift	331
7.6.1.4	Common-Mode Input Swing	331
7.6.1.5	Differential Mode Gain	331
7.6.1.6	Common-Mode Gain	331
7.6.1.7	Common-Mode Rejection Ratio	332
7.6.1.8	Power Supply Rejection Ratio	332
7.6.1.9	Input Impedance	332
7.6.1.10	Output Impedance	332
7.6.1.11	Input Bias Current	332
7.6.1.12	Gain-Bandwidth Product (Unity Gain Frequency)	333
7.6.1.13	Critical Frequency	333
7.6.1.14	Slew Rate of the Output Voltage	333
7.6.1.15	Equivalent Circuit of the Operational Amplifier	333
7.6.2	Frequency Compensation	334
7.6.3	Comparators	335
7.6.4	Circuits with Operational Amplifiers	335
7.6.4.1	Impedance Converter (follower)	336
7.6.4.2	Noninverting Amplifier	336
7.6.4.3	Inverting Amplifier	337
7.6.4.4	Summing Amplifier	338
7.6.4.5	Difference Amplifier	339
7.6.4.6	Instrumentation Amplifier	340
7.6.4.7	Voltage-Controlled Current Source	341
7.6.4.8	Integrator	341
7.6.4.9	Differentiator	342
7.6.4.10	AC Voltage Amplifier with Single-Rail Supply	343
7.6.4.11	Voltage Setting with Defined Slew Rate	343
7.6.4.12	Schmitt Trigger	344
7.6.4.13	Triangle- and Square-Wave Generator	345
7.6.4.14	Multivibrator	346
7.6.4.15	Sawtooth Generator	346
7.6.4.16	Pulse-Width Modulator	346
7.7	Active Filters	348
7.7.1	Low-Pass Filters	349
7.7.1.1	Theory of Low-Pass Filters	349
7.7.1.2	Low-Pass Filter Calculations	356
7.7.1.3	Low-Pass Filter Circuits	357
7.7.2	High-Pass Filters	359
7.7.2.1	Theory of High-Pass Filters	359
7.7.2.2	High-Pass Filter Circuits	359
7.7.3	Bandpass Filters	361
7.7.3.1	Second-Order Bandpass Filter	361
7.7.3.2	Second-Order Bandpass Filter Circuit	362
7.7.3.3	Fourth- and Higher-Order Bandpass Filters	362
7.7.4	Universal Filter	363
7.7.5	Switched-Capacitor Filter	363
7.8	Oscillators	364
7.8.1	RC Oscillators	365
7.8.1.1	Phase-Shift Oscillator	365
7.8.1.2	Wien Bridge Oscillator	366
7.8.2	LC Tuned Oscillators	367
7.8.2.1	Meissner Oscillator	367
7.8.2.2	Hartley Oscillator	367

7.8.2.3	Colpitts Oscillator	368
7.8.3	Quartz/Crystal Oscillators	368
7.8.3.1	Pierce Oscillator	369
7.8.3.2	Quartz Oscillator with TTL Gates	370
7.8.4	Multivibrators	370
7.9	Heating and Cooling	370
7.9.1	Reliability and Lifetime	371
7.9.2	Temperature Calculation	373
7.9.2.1	Thermal Resistance	373
7.9.2.2	Thermal Capacity	374
7.9.2.3	Transient Thermal Impedance	375
7.10	Power Amplifiers	376
7.10.1	Emitter Follower	376
7.10.2	Complementary Emitter Follower in Class B Operation	379
7.10.3	Complementary Emitter Follower in Class C Operation	382
7.10.4	The Characteristic Curves of the Operation Classes	383
7.10.5	Complementary Emitter Follower in Class AB Operation	383
7.10.5.1	Biasing for Class AB Operation	384
7.10.5.2	Complementary Emitter Follower with Darlington Transistors	385
7.10.5.3	Current-Limiting Complementary Emitter Follower	386
7.10.6	Input Signal Injection to Power Amplifiers	386
7.10.6.1	Input Signal Injection using a Differential Amplifier	386
7.10.6.2	Input Signal Injection Using an Op-Amp	388
7.10.7	Switched-Mode Amplifiers	388
7.11	Notation Index	389
7.12	Further Reading	390

**8 Digital Electronics 392**

8.1	Logic Algebra	392
8.1.1	Logic Variables and Logic Gates	392
8.1.1.1	Inversion	392
8.1.1.2	AND Function	392
8.1.1.3	OR Function	393
8.1.2	Logic Functions and their Symbols	393
8.1.2.1	Inverter (NOT)	394
8.1.2.2	AND Gate	394
8.1.2.3	OR Gate	394
8.1.2.4	NAND Gate	395
8.1.2.5	NOR Gate	395
8.1.2.6	XOR Gate, Exclusive OR	396
8.1.3	Logic Transformations	396
8.1.3.1	Commutative Laws	396
8.1.3.2	Associative Laws	397
8.1.3.3	Distributive Laws	397
8.1.3.4	Inversion Laws (DeMorgan's Rules)	398
8.1.4	Overview: Logic Transformations	398
8.1.5	Analysis of Logic Circuits	399
8.1.6	Sum of Products and Product of Sums	400
8.1.6.1	Sum of Products	400
8.1.6.2	Product of Sums	401
8.1.7	Systematic Reduction of a Logic Function	402
8.1.7.1	Karnaugh Map	402
8.1.7.2	The Quine–McCluskey Technique	406

---

8.1.8	Synthesis of Combinational Circuits . . . . .	408
8.1.8.1	Implementation Using only NAND Gates . . . . .	408
8.1.8.2	Implementation Using only NOR Gates . . . . .	408
8.2	Electronic Realisation of Logic Circuits . . . . .	409
8.2.1	Electrical Specification . . . . .	409
8.2.1.1	Voltage Levels . . . . .	409
8.2.1.2	Transfer Characteristic . . . . .	409
8.2.1.3	Loading . . . . .	410
8.2.1.4	Noise Margin . . . . .	410
8.2.1.5	Propagation Delay Time . . . . .	411
8.2.1.6	Rise Times . . . . .	411
8.2.1.7	Power Loss . . . . .	412
8.2.1.8	Minimum Slew Rate . . . . .	412
8.2.1.9	Integration . . . . .	412
8.2.2	Overview: Notation in Data Sheets . . . . .	412
8.2.3	TTL Family . . . . .	414
8.2.3.1	TTL Devices . . . . .	414
8.2.3.2	Basic TTL Gate Circuit . . . . .	416
8.2.4	CMOS Family . . . . .	417
8.2.5	Comparison of TTL and CMOS . . . . .	418
8.2.5.1	Other Logic Families . . . . .	418
8.2.6	Special Circuit Variations . . . . .	420
8.2.6.1	Outputs with Open Collector . . . . .	420
8.2.6.2	Wired AND/OR . . . . .	420
8.2.6.3	Tri-State Outputs . . . . .	422
8.2.6.4	Schmitt Trigger Inputs . . . . .	422
8.3	Combinational Circuits and Sequential Logic . . . . .	423
8.3.1	Dependency Notation . . . . .	423
8.3.1.1	Overview: Dependency Notation . . . . .	425
8.3.2	Circuit Symbols for Combinational and Sequential Logic . . . . .	425
8.4	Examples of Combinational Circuits . . . . .	426
8.4.1	1-to- $n$ Decoder . . . . .	426
8.4.2	Multiplexer and Demultiplexer . . . . .	426
8.4.2.1	Overview of Circuits . . . . .	428
8.5	Latches and Flip-Flops . . . . .	428
8.5.1	Flip-Flop Applications . . . . .	428
8.5.2	SR Flip-Flop . . . . .	429
8.5.2.1	SR Flip-Flop with Clock Input . . . . .	430
8.5.3	D Flip-Flop . . . . .	430
8.5.4	Master-Slave Flip-Flop . . . . .	431
8.5.5	JK Flip-Flop . . . . .	432
8.5.6	Flip-Flop Triggering . . . . .	432
8.5.7	Notation for Flip-Flop Circuit Symbols . . . . .	433
8.5.8	Overview: Flip-Flops . . . . .	434
8.5.9	Overview: Edge-Triggered Flip-Flops . . . . .	434
8.5.10	Synthesis of Edge-Triggered Flip-Flops . . . . .	436
8.5.11	Overview: Flip-Flop Circuits . . . . .	438
8.6	Memory . . . . .	439
8.6.1	Memory Construction . . . . .	439
8.6.2	Memory Access . . . . .	440
8.6.3	Static and Dynamic RAMs . . . . .	441
8.6.3.1	Variations of RAM . . . . .	442
8.6.4	Read-Only Memory . . . . .	443
8.6.5	Programmable Logic Devices . . . . .	444

8.6.5.1	Principle of Operation . . . . .	444
8.6.5.2	PLD Types . . . . .	445
8.6.5.3	Output Circuits . . . . .	446
8.7	Registers and Shift Registers . . . . .	448
8.8	Counters . . . . .	449
8.8.1	Asynchronous Counters . . . . .	450
8.8.1.1	Binary Counter . . . . .	450
8.8.1.2	Decimal Counter . . . . .	450
8.8.1.3	Down Counter . . . . .	453
8.8.1.4	Up/Down Counter . . . . .	454
8.8.1.5	Programmable Counter . . . . .	454
8.8.2	Synchronous Counters . . . . .	455
8.8.2.1	Cascading Synchronous Counters . . . . .	456
8.8.3	Overview: TTL and CMOS Counters . . . . .	458
8.8.3.1	TTL Counters . . . . .	459
8.8.3.2	CMOS Counters . . . . .	459
8.9	Design and Synthesis of Sequential Logic . . . . .	460
8.10	Further Reading . . . . .	467
<b>9</b>	<b>Power Supplies</b> . . . . .	<b>469</b>
9.1	Power Transformers . . . . .	469
9.2	Rectification and Filtering . . . . .	470
9.2.1	Different Rectifier Circuits . . . . .	472
9.3	Analogue Voltage Stabilisation . . . . .	473
9.3.1	Voltage Stabilisation with Zener Diode . . . . .	473
9.3.2	Analogue Stabilisation with Transistor . . . . .	474
9.3.3	Voltage Regulation . . . . .	475
9.3.3.1	Integrated Voltage Regulators . . . . .	475
9.4	Switched Mode Power Supplies . . . . .	476
9.4.1	Single-Ended Converters, Secondary Switched SMPS . . . . .	477
9.4.1.1	Buck Converter . . . . .	477
9.4.1.2	Boost Converter . . . . .	479
9.4.1.3	Buck-Boost Converter . . . . .	481
9.4.2	Primary Switched SMPS . . . . .	482
9.4.2.1	Flyback Converter . . . . .	482
9.4.2.2	Single-Transistor Forward Converter . . . . .	486
9.4.2.3	Push–Pull Converters . . . . .	489
9.4.2.4	Resonant Converters . . . . .	491
9.4.3	Overview: Switched-Mode Power Supplies . . . . .	494
9.4.4	Control of Switched-Mode Power Supplies . . . . .	496
9.4.4.1	Voltage-Mode Control . . . . .	496
9.4.4.2	Current-Mode Control . . . . .	497
9.4.4.3	Comparison: Voltage-Mode vs. Current-Mode Control . . . . .	498
9.4.4.4	Design of the PI Controller . . . . .	498
9.4.5	Design of Inductors and High-Frequency Transformers . . . . .	499
9.4.5.1	Calculation of Inductors . . . . .	499
9.4.5.2	Calculation of High-Frequency Transformers . . . . .	500
9.4.6	Power Factor Control . . . . .	504
9.4.6.1	Currents, Voltages and Power of the PFC . . . . .	505
9.4.6.2	Controlling the PFC . . . . .	506
9.4.7	Radio-Frequency Interference Suppression of Switched-Mode Power Supplies . . . . .	507
9.4.7.1	Radio-Frequency Interference Radiation . . . . .	507
9.4.7.2	Mains Input Conducted-Mode Interference . . . . .	508

9.4.7.3	Suppression of Common-Mode Radio-Frequency Interference	509
9.4.7.4	Suppression of Differential-Mode Radio Frequency Interference	509
9.4.7.5	Complete Radio-Frequency Interference Filter	510
9.5	Notation Index	511
9.6	Further Reading	512
<b>A</b>	<b>Mathematical Basics</b>	<b>513</b>
A.1	Trigonometric Functions	513
A.1.1	Properties	513
A.1.2	Sums and Differences of Trigonometric Functions	514
A.1.3	Sums and Differences in the Argument	515
A.1.4	Multiples of the Argument	515
A.1.5	Weighted Sums of Trigonometric Functions	516
A.1.6	Products of Trigonometric Functions	516
A.1.7	Triple Products	516
A.1.8	Powers of Trigonometric Functions	517
A.1.9	Trigonometric Functions with Complex Arguments	517
A.2	Inverse Trigonometric Functions (Arc Functions)	517
A.3	Hyperbolic Functions	518
A.4	Differential Calculus	518
A.4.1	Basics of Differential Calculus	518
A.4.2	Derivatives of Elementary Functions	519
A.5	Integral Calculus	519
A.5.1	Basics of Integral Calculus	519
A.5.1.1	Integrals of Elementary Functions	520
A.5.2	Integrals Involving Trigonometric Functions	521
A.5.3	Integrals Involving Exponential Functions	523
A.5.4	Integrals Involving Inverse Trigonometric Functions	524
A.5.5	Definite Integrals	524
A.6	The Integral of the Standard Normal Distribution	527
<b>B</b>	<b>Tables</b>	<b>530</b>
B.1	The International System of Units (SI)	530
B.1.1	Decimal Prefixes	531
B.1.2	SI Units in Electrical Engineering	532
B.2	Naturally Occurring Constants	533
B.3	Symbols of the Greek Alphabet	533
B.4	Units and Definitions of Technical–Physical Quantities	534
B.5	Imperial and American Units	535
B.6	Other Units	537
B.7	Charge and Discharge Curves	540
B.8	IEC Standard Series	541
B.9	Resistor Colour Code	542
B.10	Parallel Combination of Resistors	543
B.11	Selecting Track Dimensions for Current Flow	544
B.12	American Wire Gauge	545
B.13	Dry Cell Batteries	546
B.14	Notation of Radio-Frequency Ranges	548
B.15	Ratios	549
B.15.1	Absolute Voltage Levels	549
B.15.1.1	Conversion of Power and Voltage Level Ratios	550
B.15.2	Relative Levels	551

B.16 V.24 Interface . . . . .	552
B.17 Dual-Tone Multi-Frequency . . . . .	553
B.18 ASCII Coding . . . . .	554
B.19 Resolution and Coding for Analogue-to-Digital Converters . . . . .	555
B.20 Chemical Elements . . . . .	556
B.21 Materials . . . . .	559
<b>C Acronyms</b>	<b>561</b>
<b>D Circuit Symbols</b>	<b>595</b>
<b>Index</b>	<b>601</b>