

# Contents

## Part I Theory

<b>1</b>	<b>Amps, Pre-Amps, Pre-Pre-Amps</b>	3
<b>2</b>	<b>RIAA Transfer/Anti-RIAA Transfer</b>	9
<b>3</b>	<b>Noise Basics</b>	17
3.1	Noise in Components and Other General Noise Effects	17
3.2	Noise in Bipolar Junction Transistors (BJTs)	36
3.3	Noise in Field Effect Transistors (FETs)	55
3.4	Noise in Valves (US: Tubes)	71
3.5	Noise in Operational Amplifiers (Op-Amps)	86
3.6	Noise in Instrumentation Amps (In-Amps)	93
3.7	Noise in Transformers (Trafos)	106
3.8	Noise of Vinyl Records (VRs) – On how much Phono-Amp SN is Needed?	125

## Part II Best Practice

<b>4</b>	<b>Noise in MM Cartridges</b>	149
<b>5</b>	<b>Noise in MM Cartridges – Mathematical Calculation Course</b>	171
<b>6</b>	<b>Noise in MC Phono-Amps</b>	181
<b>7</b>	<b>Noise in MC Phono-Amps – Mathematical Calculation Course</b>	205
<b>8</b>	<b>RIAA Networks</b>	227
<b>9</b>	<b>RIAA Networks – Mathematical Calculation Course</b>	255

**Part III Noise Measurement System**

<b>10 System Overview</b> .....	279
<b>11 Measurement Amps</b> .....	285
<b>12 Measurement Filters and Networks</b> .....	291

**Part IV The RIAA Phono-Amp Engine**

<b>13 Overview</b> .....	303
<b>14 Module 1</b> .....	309
<b>15 Module 2</b> .....	311
<b>16 Module 3</b> .....	313
<b>17 Engine Performance</b> .....	319

**Part V Book-Ending Sections**

<b>List of Figures</b> .....	329
<b>List of Tables</b> .....	339
<b>Constants, Abbreviations, Symbols</b> .....	341
<b>Index</b> .....	345
<b>Epilogue</b> .....	351